

**INDIAN INSTITUTE OF TECHNOLOGY, KANPUR**

**EE-619 VLSI SYSTEM DESIGN**

**VERILOG PROJECT**

**GROUP NO: 7**

**ANANYA 190126**

**ADITI 190055**


**MADIHA FATIMA 19807465**

**SAI VEDANT-210901**

**Course Instructor : Dr. Rik Dey**

- **Icarus Verilog and gtkwave can be used to simulate all the circuits designed.**
- **All the simulation files are present in the folder itself.**
- **Commands to run the simulations are given along with each part.**

**Q1 a)**

 

S	Out
0	B
1	A

(b)

A	B	S	Out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(c)

- Structural modelling of 2-to-1 Multiplexer

**Verilog file:** mux2s.v


**Testbench:** mux2s\_tb.v

**Command to run testbench:**

```
$ iverilog -o mux2s_tb.vvp mux2s_tb.v
```

```
$ vvp mux2s_tb.vvp
```

**gtkwave file:** mux2s\_tb.vcd

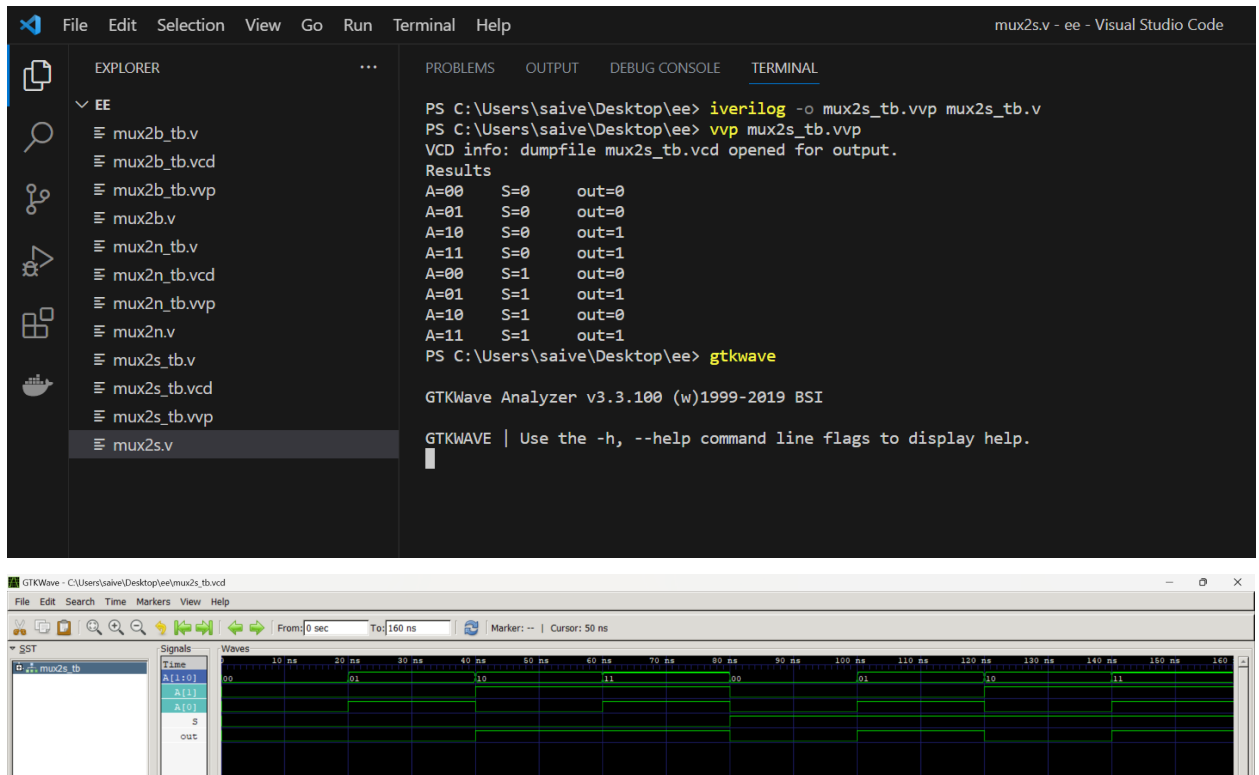

## ● Behavioral modelling of 2-to-1 Multiplexer

**Verilog file:** mux2b.v

**Testbench:** mux2b\_tb.v

**Command to run testbench:**

```
$ iverilog -o mux2b_tb.vvp mux2b_tb.v
```


```
$ vvp mux2b_tb.vvp
```

**gtkwave file:** mux2b\_tb.vcd

```

PS C:\Users\saive\Desktop\ee> iverilog -o mux2b_tb.vvp mux2b_tb.v
PS C:\Users\saive\Desktop\ee> vvp mux2b_tb.vvp
VCD info: dumpfile mux2b_tb.vcd opened for output.
Results
A=00    S=0    out=0
A=00    S=1    out=0
A=01    S=0    out=0
A=01    S=1    out=1
A=10    S=0    out=1
A=10    S=1    out=0
A=11    S=0    out=1
A=11    S=1    out=1
A=00    S=0    out=0
A=00    S=1    out=0
A=01    S=0    out=0
A=01    S=1    out=1
A=10    S=0    out=1
A=10    S=1    out=0
A=11    S=0    out=1
A=11    S=1    out=1
A=00    S=0    out=0
A=00    S=1    out=0
A=01    S=0    out=0
A=01    S=1    out=1
mux2b_tb.v:18: $finish called at 100 (1ns)
PS C:\Users\saive\Desktop\ee>

```

 

- 2n-to-1 Multiplexer using 2-to-1 Multiplexer and implementation of 5 variable function

**Verilog file:** mux2n.v

**Testbench:** mux2n\_tb.v

**Command to run testbench:**

```
$ iverilog -o mux2n_tb.vvp mux2n_tb.v
```


```
$ vvp mux2n_tb.vvp
```

**gtkwave file:** mux2n\_tb.vcd


**32-to-1 multiplexer was implemented using the 2-to-1 multiplexer designed above. As an example the arbitrary function**

**$F = ABCDE + A'B'C'D'E'$  was implemented in the testbench.**

## Results

 [illegible]

Q1 b)

 

**Truth table of JK flip-flop**

C	J	K	Q	Q'
HIGH	0	0	Latch	Latch
HIGH	0	1	0	1
HIGH	1	0	1	0
HIGH	1	1	Toggle	Toggle
LOW	0	0	Latch	Latch
LOW	0	1	Latch	Latch
LOW	1	0	Latch	Latch
LOW	1	1	Latch	Latch

- Behavioral modelling of JK Flip Flop

**Verilog file:** jkb.v

**Testbench:** jkb\_tb.v

**Command to run testbench:**


```
$ iverilog -o jkb_tb.vvp jkb_tb.v
```

```
$ vvp jkb_tb.vvp
```

**gtkwave file:** jkb\_tb.vcd

```
PS C:\Users\saive\Desktop\Verilog Project EE619A Group 7> iverilog -o jkb_tb.vvp jkb_tb.v
PS C:\Users\saive\Desktop\Verilog Project EE619A Group 7> vvp jkb_tb.vvp
VCD info: dumpfile jkb_tb.vcd opened for output.
j=x      k=x      q=0      qbar=1
j=x      k=x      q=0      qbar=1
j=0      k=0      q=0      qbar=1
j=0      k=1      q=0      qbar=1
j=1      k=0      q=1      qbar=0
j=1      k=1      q=0      qbar=1
jkb_tb.v:40: $finish called at 60 (1ns)
PS C:\Users\saive\Desktop\Verilog Project EE619A Group 7> █
```



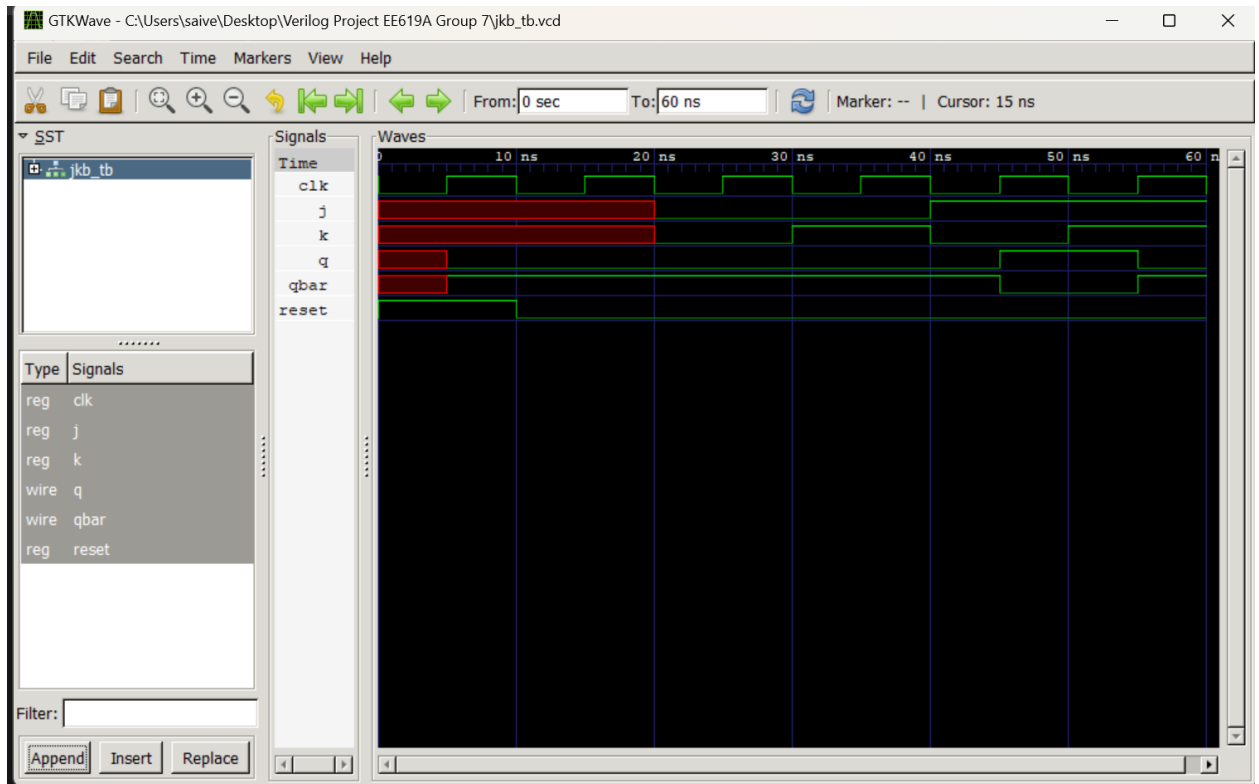

**### Values that are in Red are Undefined('x' values)**

- **Structural modelling of JK Flip Flop**

**Verilog file:** jks.v

**Testbench:** jks\_tb.v


**Command to run testbench:**

```
$ iverilog -o jks_tb.vvp jks_tb.v
```

```
$ vvp jks_tb.vvp
```

**gtkwave file:** jks\_tb.vcd

 - 4 bit synchronous counter using JK FlipFlop



Rst	CLK	O3	O2	O1	O0
1	↑	0	0	0	0
0	↑	0	0	0	1
0	↑	0	0	1	0
0	↑	0	0	1	1
0	↑	0	1	0	0
0	↑	0	1	0	1
0	↑	0	1	1	0
0	↑	0	1	1	1
0	↑	1	0	0	0
0	↑	1	0	0	1
0	↑	1	0	1	0
0	↑	1	0	1	1
0	↑	1	1	0	0
0	↑	1	1	0	1
0	↑	1	1	1	0
0	↑	1	1	1	1
0	↑	0	0	0	0

**Verilog file:** count.v

**Testbench:** count\_tb.v


**Command to run testbench:**

```
$ iverilog -o count_tb.vvp count_tb.v
```

```
$ vvp count_tb.vvp
```

**gtkwave file:** count\_tb.vcd

```
PS C:\Users\saive\Desktop\Verilog Project EE619A Group 7> iverilog -o count_tb.vvp count_tb.v
PS C:\Users\saive\Desktop\Verilog Project EE619A Group 7> vvp count_tb.vvp
VCD info: dumpfile count_tb.vcd opened for output.
0      0      0      0
0      0      0      1
0      0      1      0
0      0      1      1
0      1      0      0
0      1      0      1
0      1      1      0
0      1      1      1
1      0      0      0
1      0      0      1
1      0      1      0
1      0      1      1
1      1      0      0
1      1      0      1
1      1      1      0
1      1      1      1
0      0      0      0
0      0      0      1
0      0      1      0
0      0      1      1
0      1      0      0
0      1      0      1
0      1      1      0
0      1      1      1
1      0      0      0
1      0      0      1
1      0      1      0
1      0      1      1
1      1      0      0
1      1      0      1
1      1      1      0
1      1      1      1
count_tb.v:31: $finish called at 320 (1ns)
PS C:\Users\saive\Desktop\Verilog Project EE619A Group 7> gtkwave
```

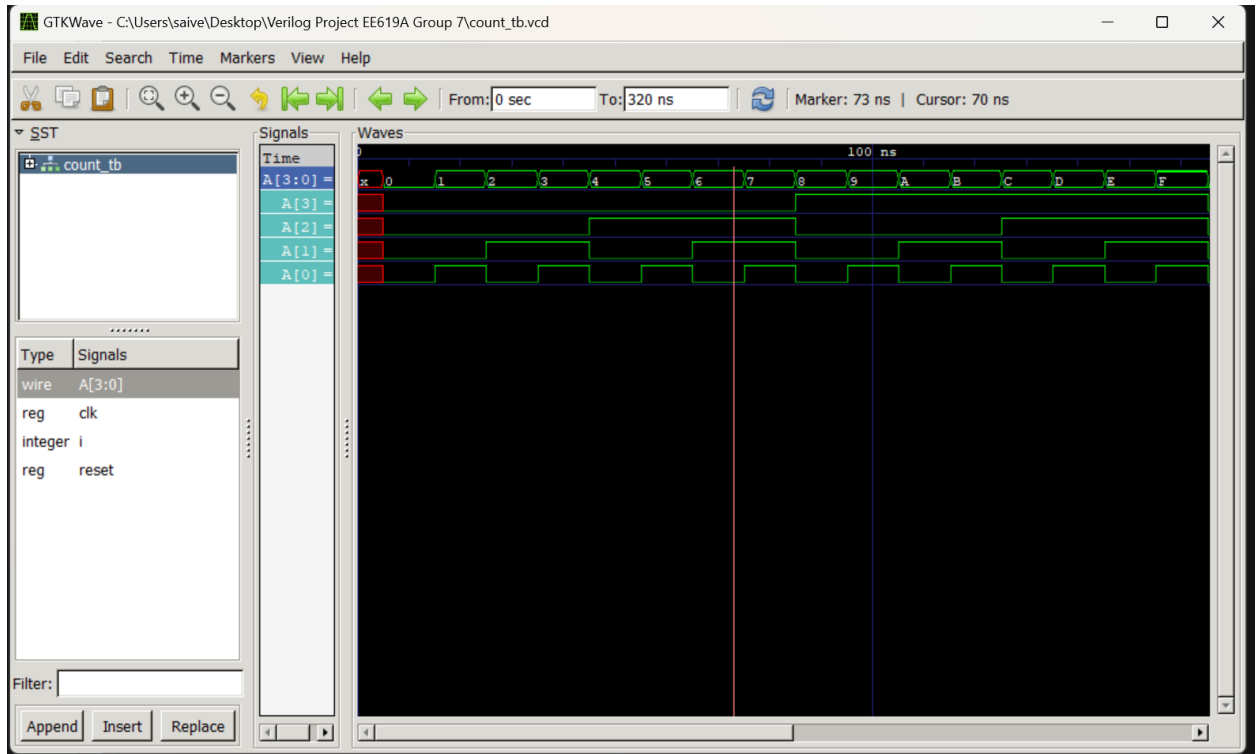

**As we can see the Register A is synchronously increasing to 15.**