

INDIAN INSTITUTE OF TECHNOLOGY,
KANPUR

EE-619 VLSI SYSTEM DESIGN

SPICE PROJECT

GROUP NO: 7

ANANYA

ADITI


MADIHA FATIMA

SAI VEDANT-210901


Course Instructor : Dr. Rik Dey

Technology used:-IBM018 (Library Files attached)


1) A) VTC of inverter

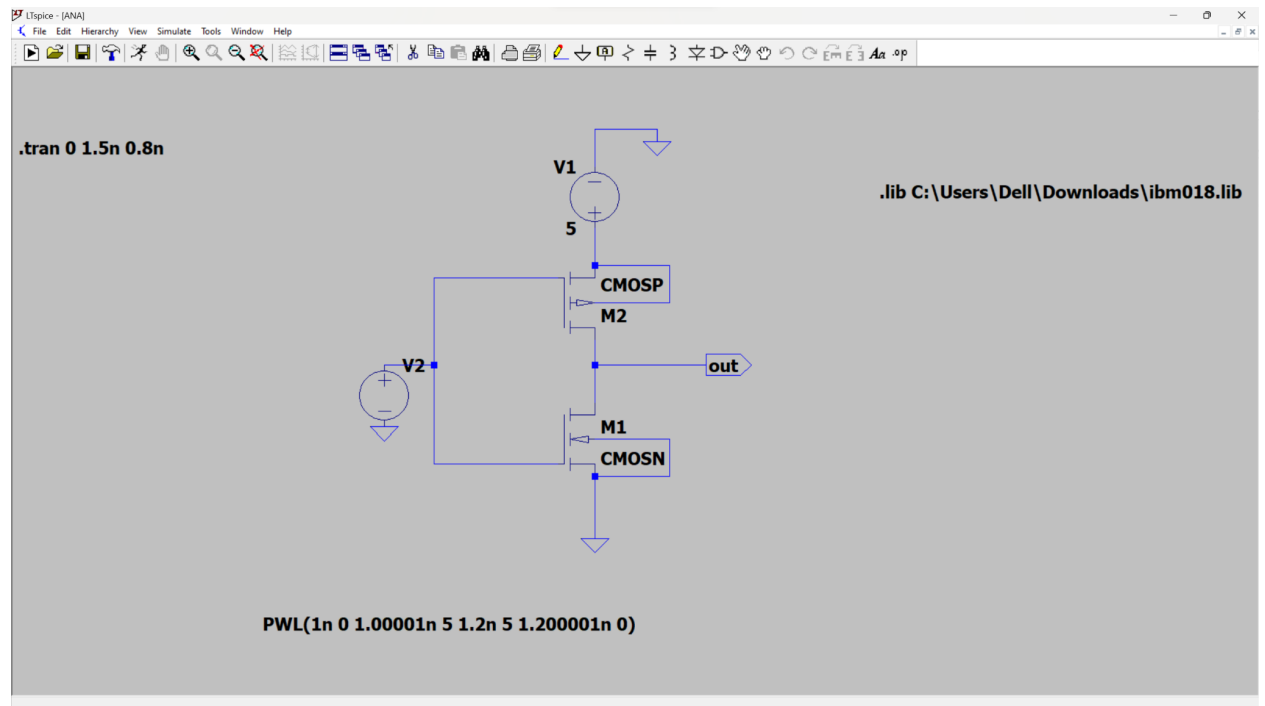

INVERTER SCHEMATIC

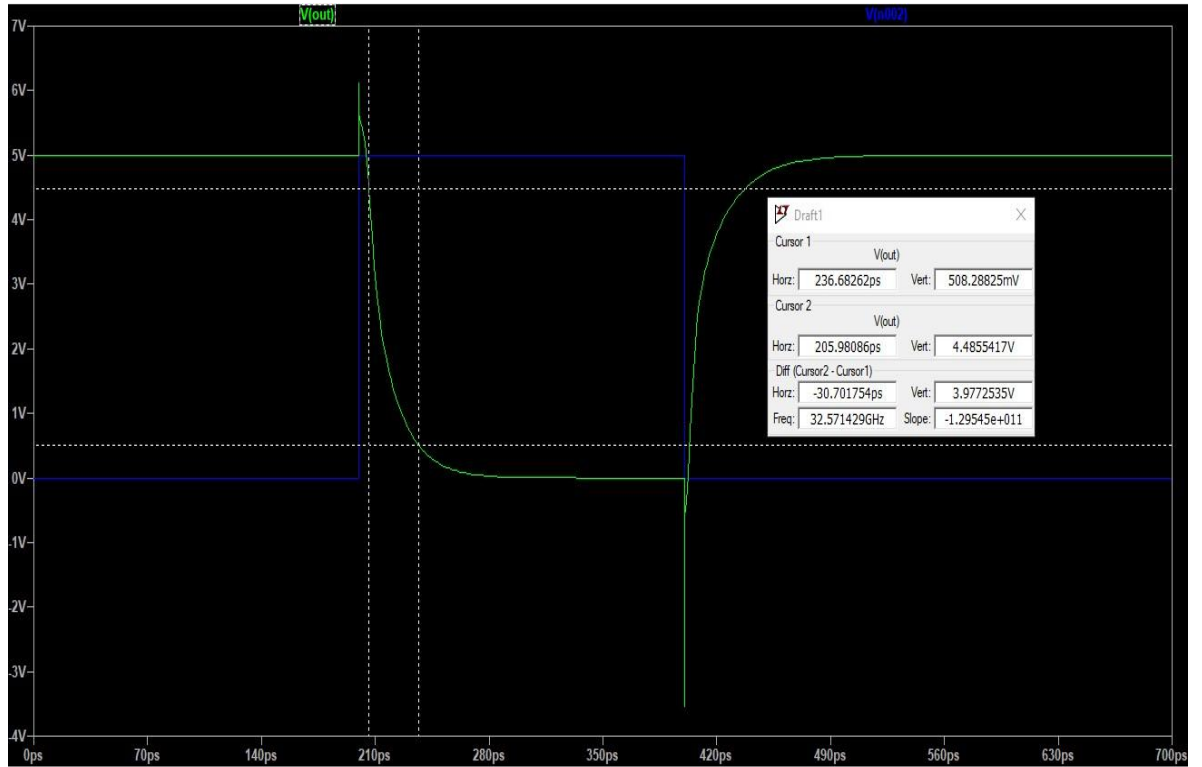

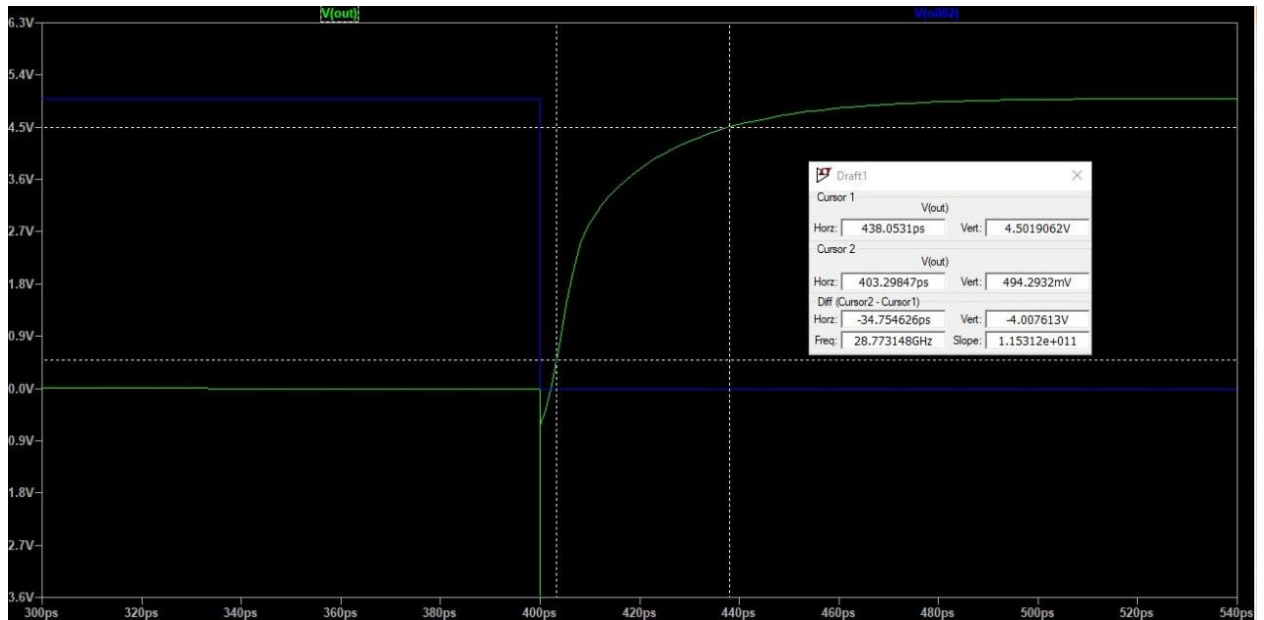Fall Time of Minimum size inverter=30.70ps




Rise Time of Minimum size inverter=34.75ps


Required sizing

NMOS(Minimum size)- $W=250\text{nm}$. $L=1000\text{nm}$. $(W/L)_n=0.25$

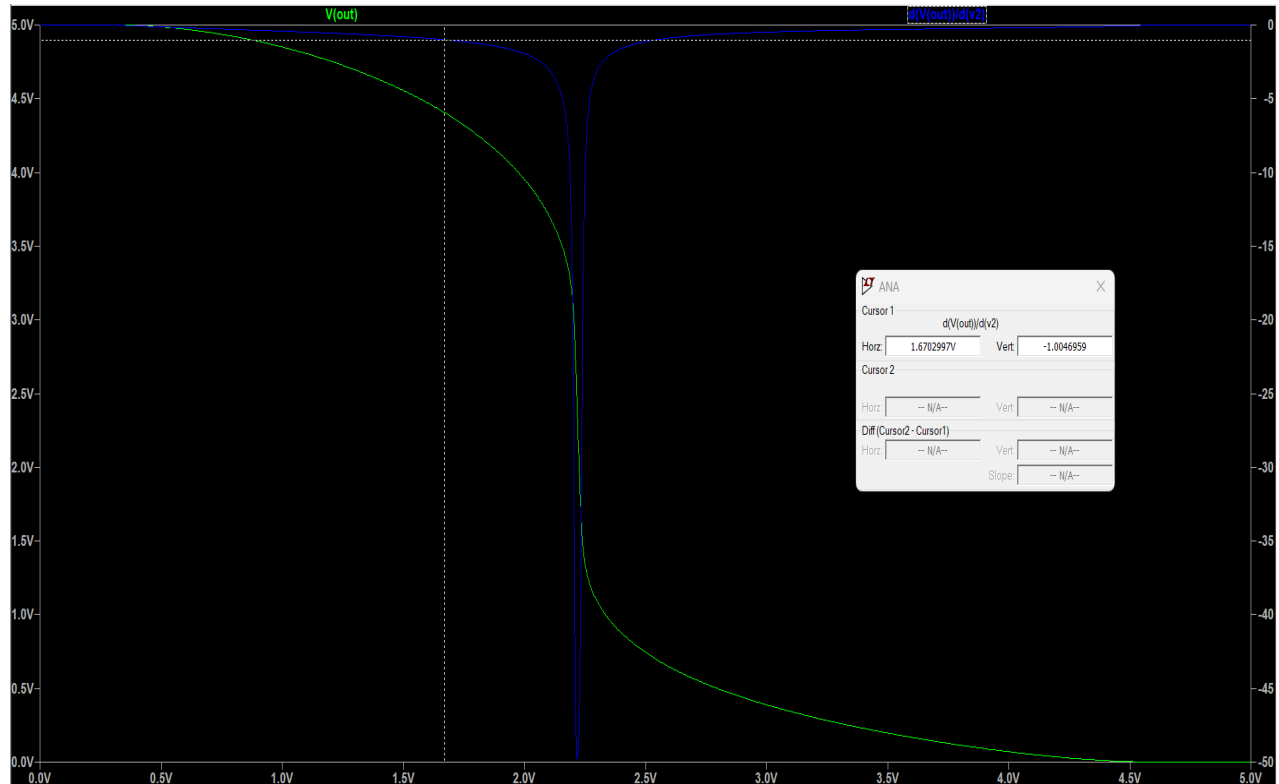
PMOS(Minimum size)- $W=518.4\text{nm}$. $L=1000\text{nm}$. $(W/L)_p=4.44$




VTC with $V_{IL}=1.67\text{V}$

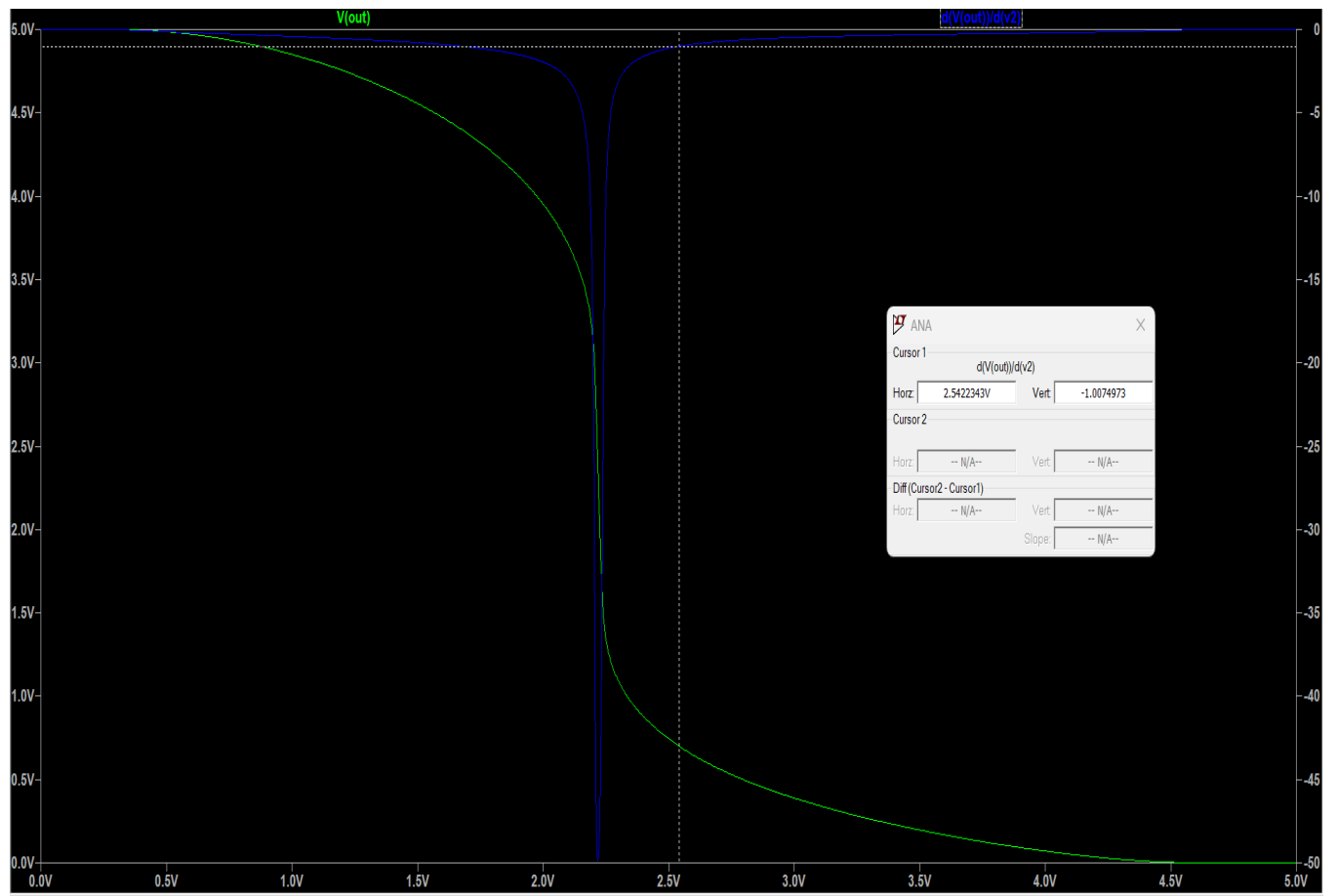

$V_{IH} = 2.54V$

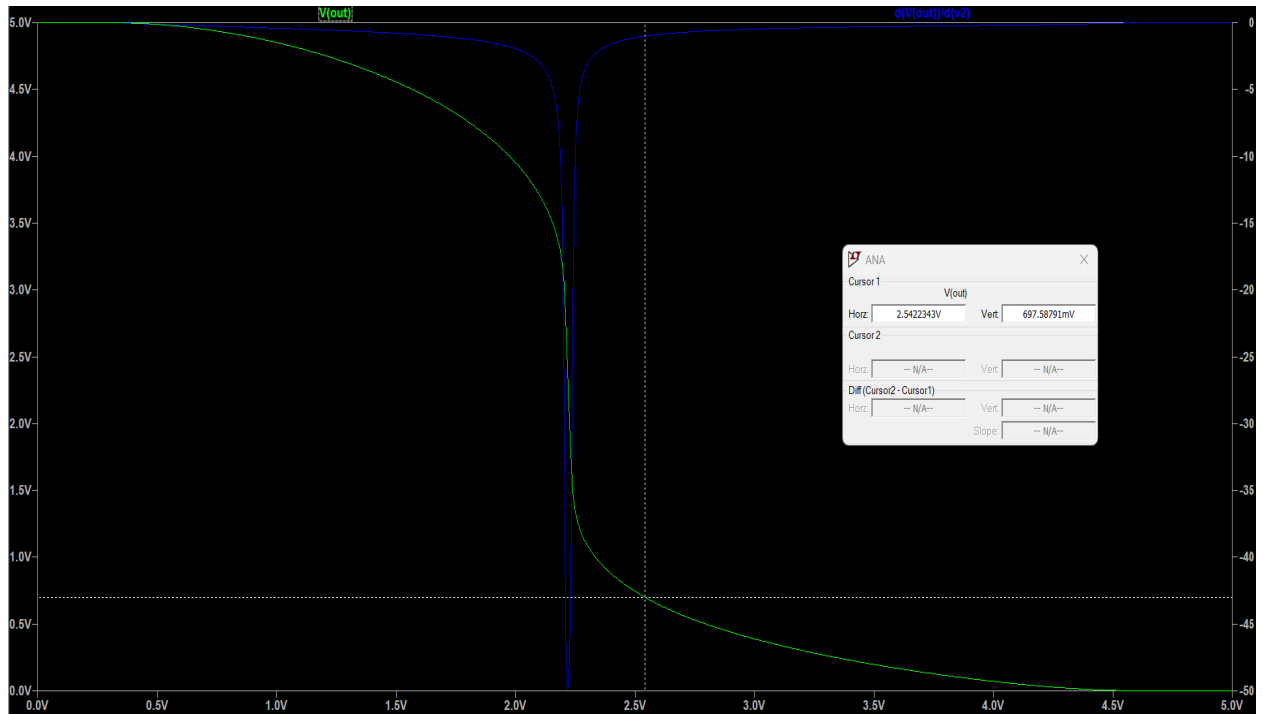

$VOL=0.69V$

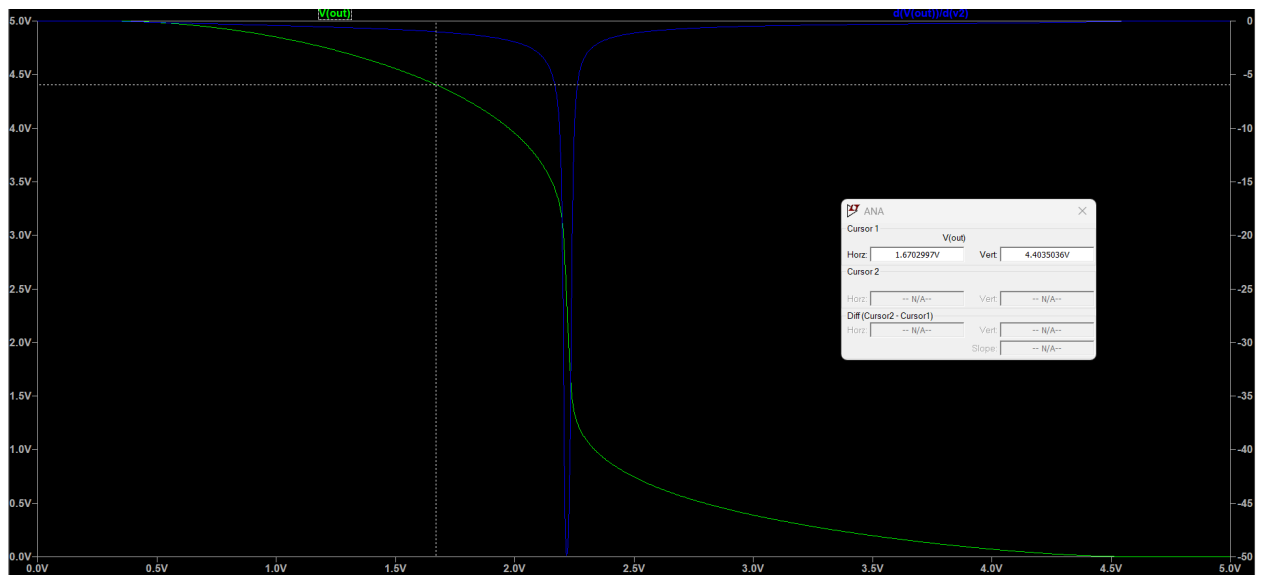


$VOH=4.40V$

$$\text{NML} = \text{VIL} - \text{VOL} = 0.98$$

$$\text{NMH} = \text{VOH} - \text{VIH} = 1.86$$
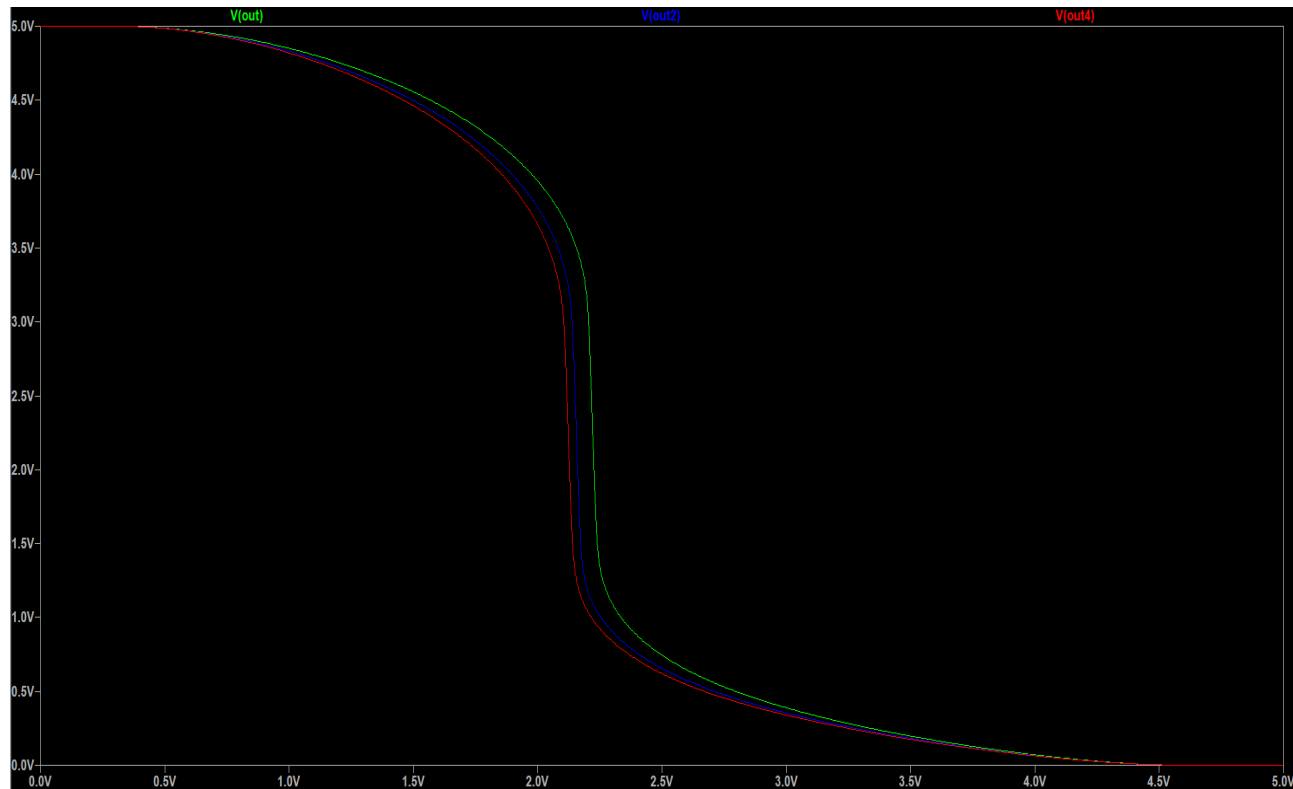
$$\text{Noise immunity} = \text{Min}(\text{NML}, \text{NMH}) = 0.98\text{V}$$




Variation of VTC with sizing.

Green S=1

Blue S=2


Red S=4

B) Transient Analysis

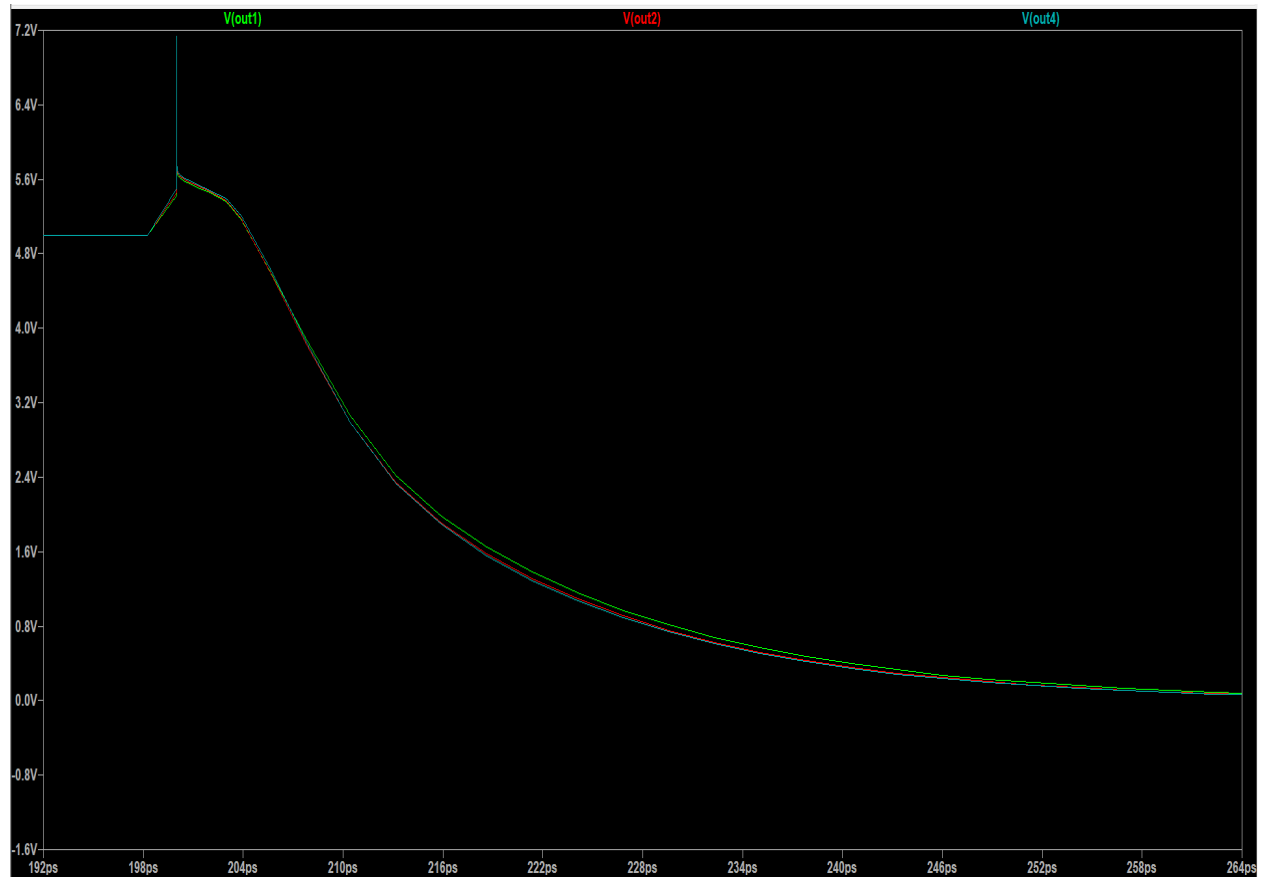


Fall time without Capacitor

Size	Fall Time(without cap)
S=1	32ps
S=2	22ps
S=4	20ps

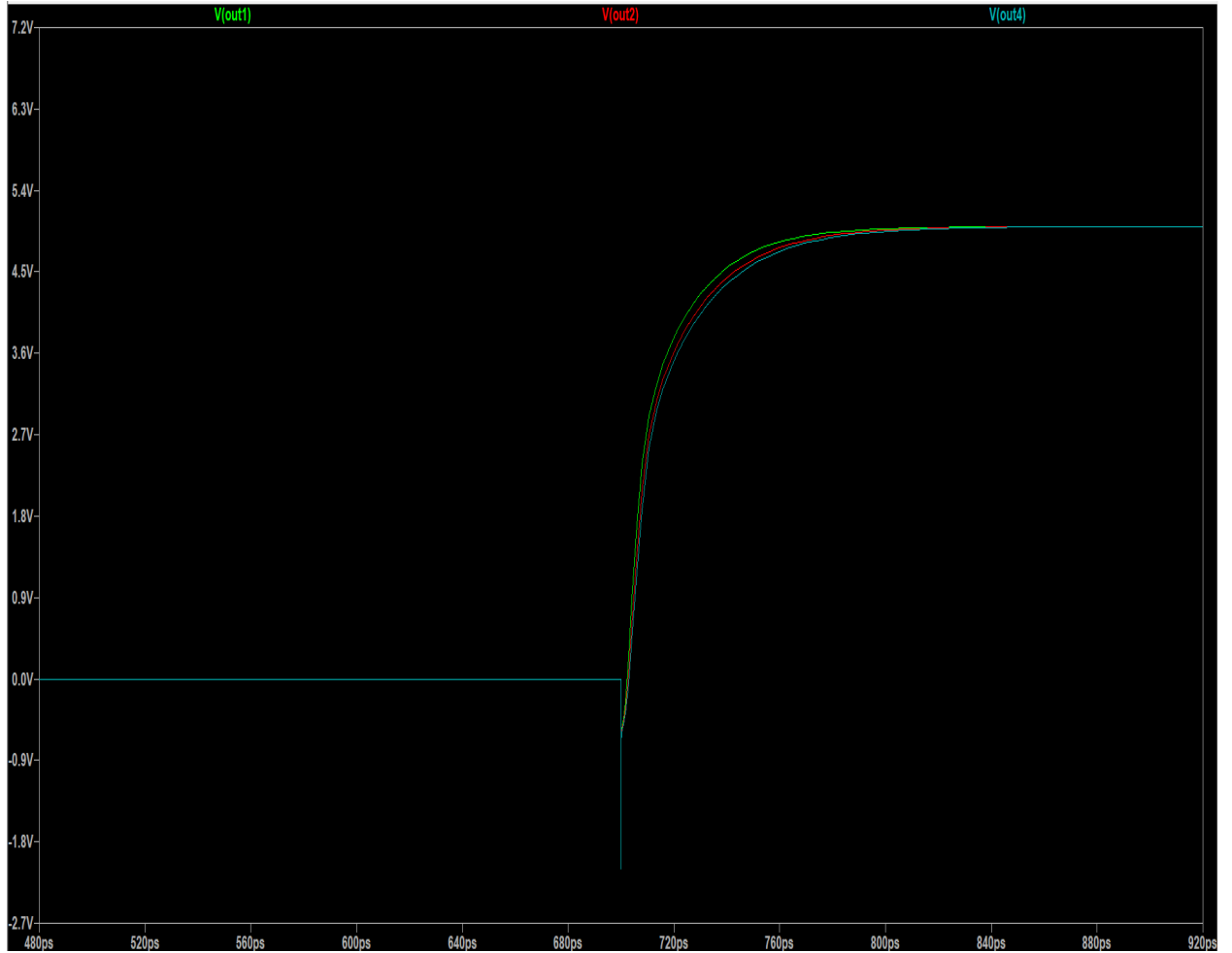


Rise time without Capacitor

Size	Rise Time(without cap)
S=1	47ps
S=2	39ps
S=4	38ps

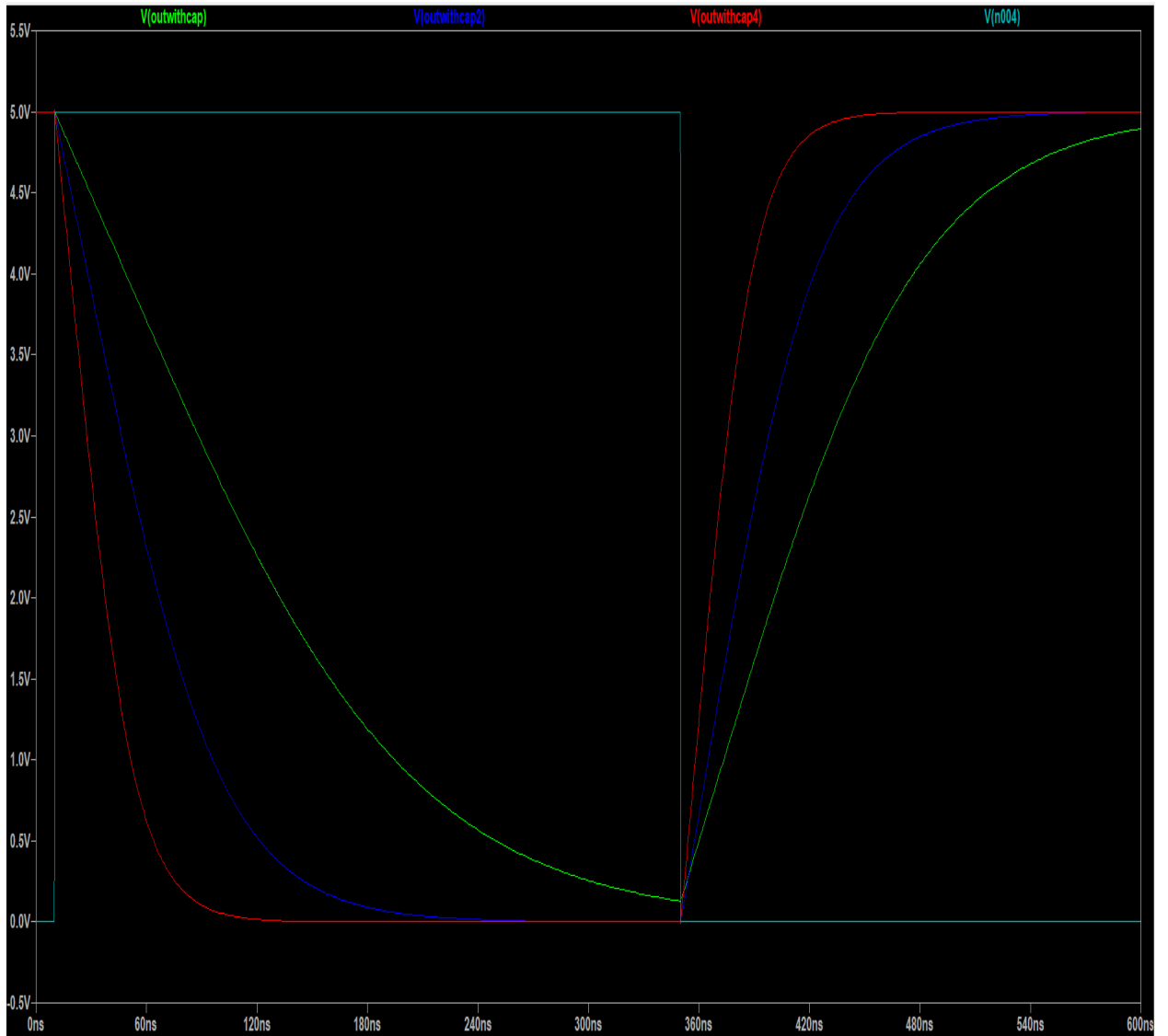

Fall and Rise time with Capacitor

Size	Fall Time(with cap)	Rise Time(with cap)
S=1	219.41ns	156.399ns
S=2	100.21ns	89.967ns
S=4	50.108ns	46.69ns

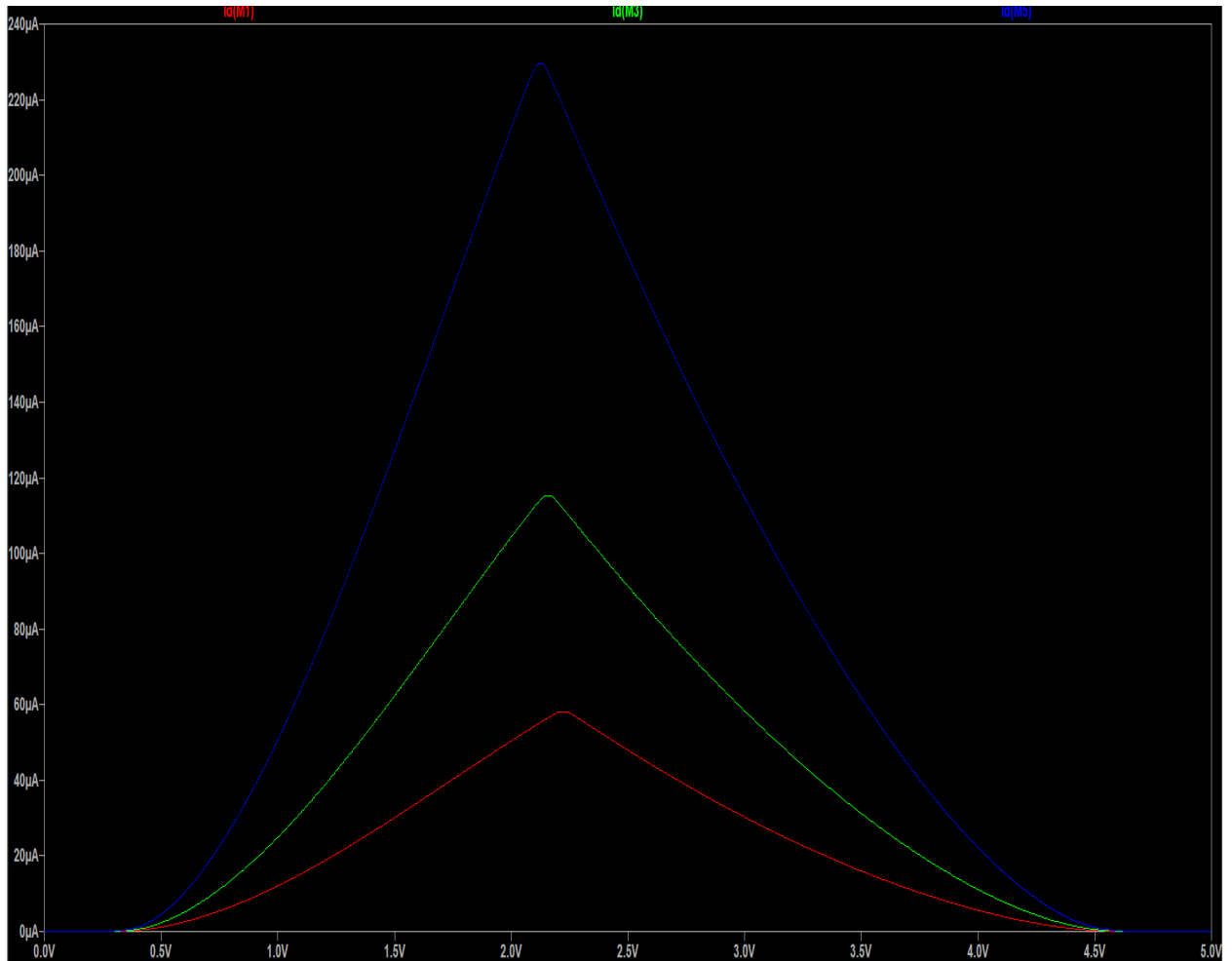


Current drawn


Power Calculations

Size	Avg Current	Static Power
1	21.92pA	109.6 pW
2	31.382pA	156.6pW
4	51.933pA	259.665pW


C)VTC of Skewed CMOS Inverter

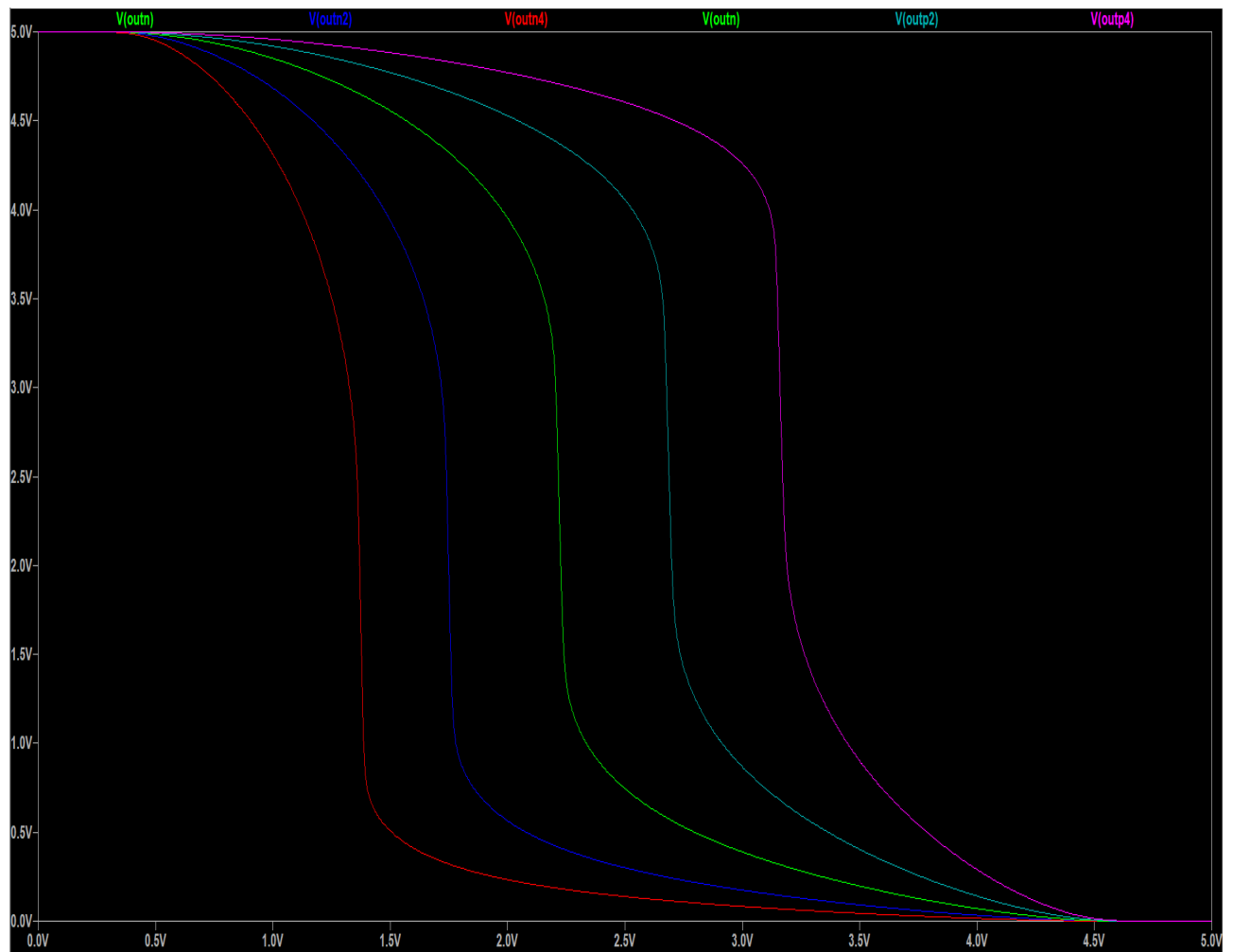

D) Transient Analysis

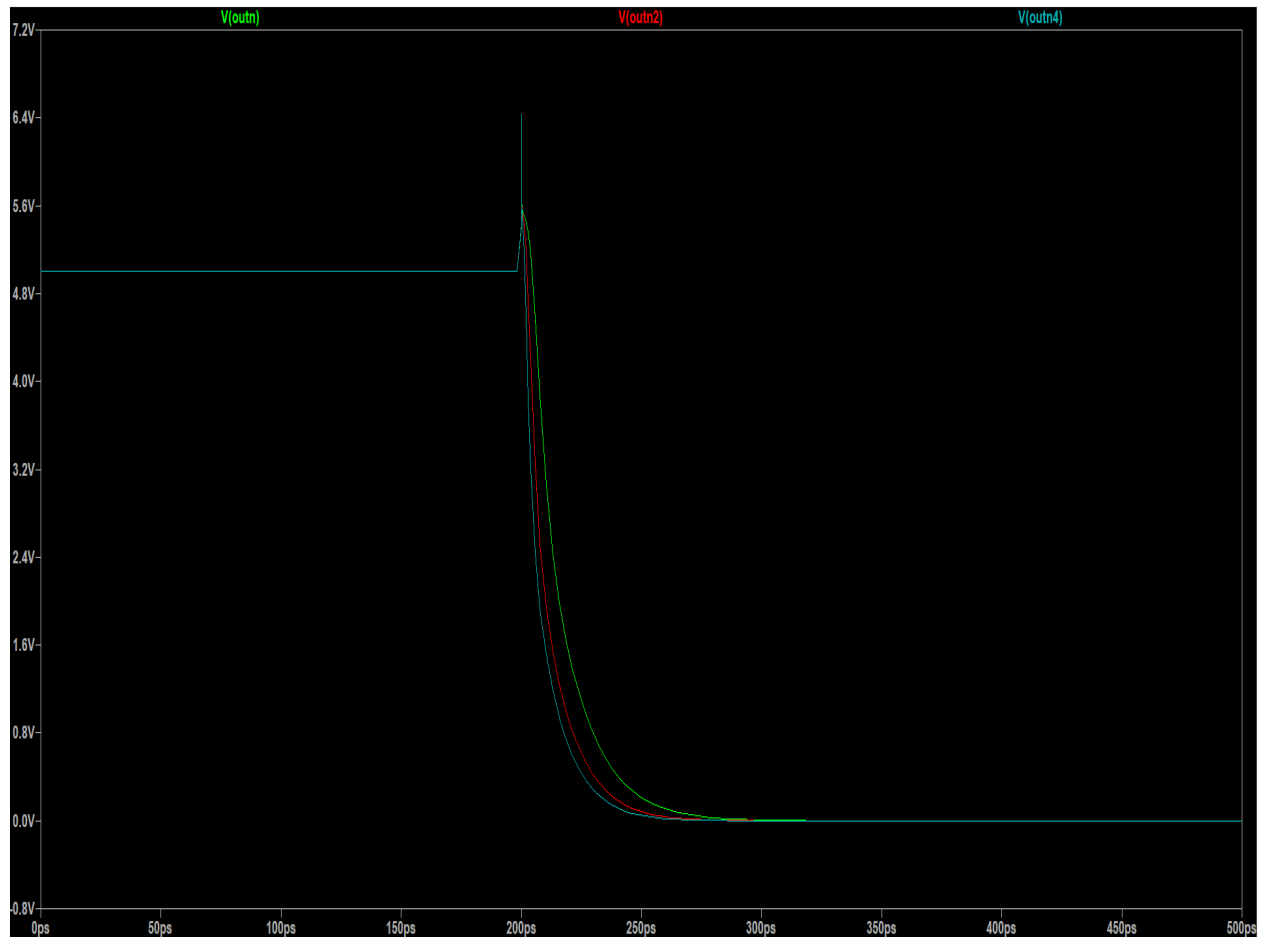


Fall time of Varying N without Capacitor

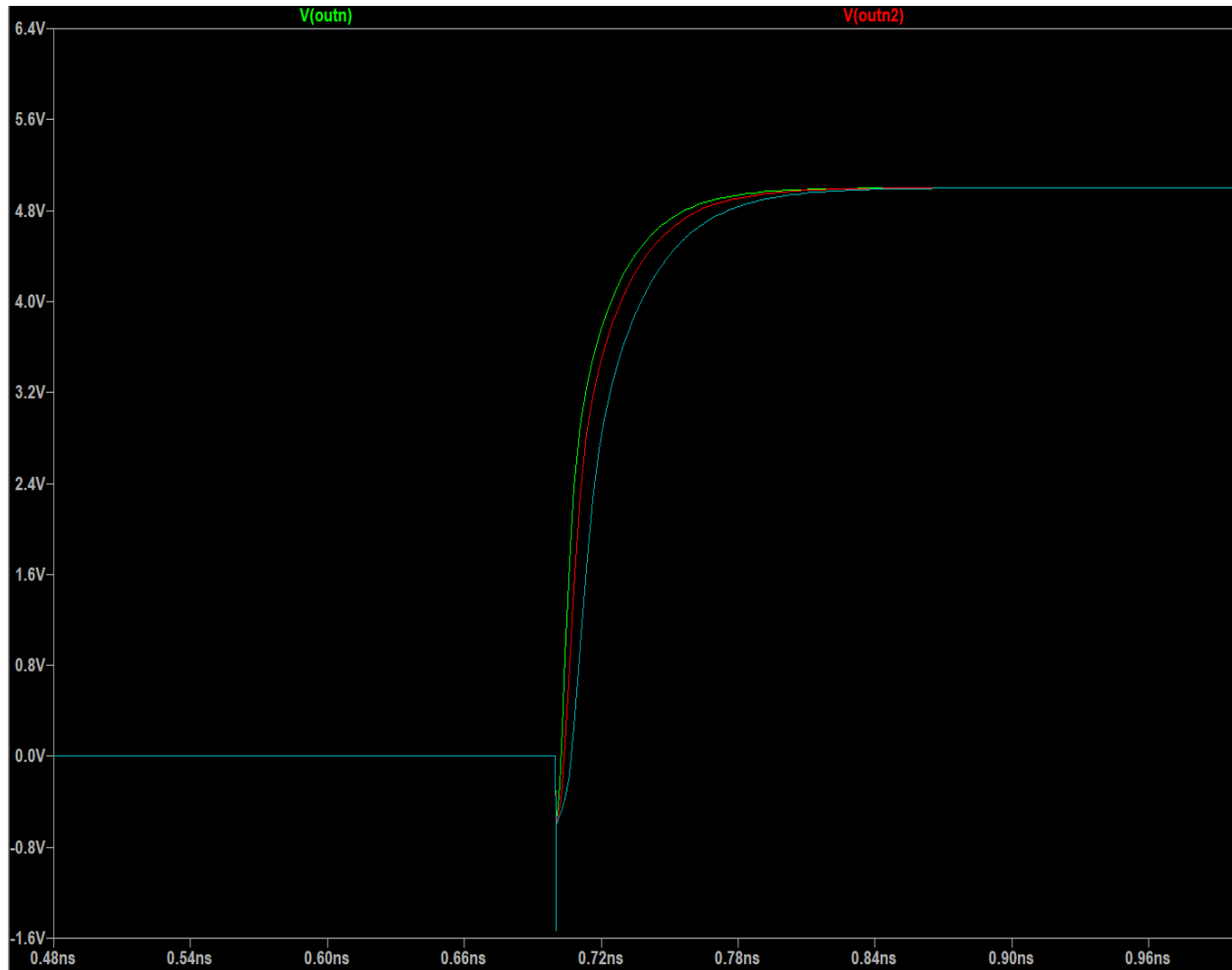


Rise Time of Varying N without Capacitor

Size	Fall Time- n without cap	Rise Time- n without cap
1	31.07ps	35.09ps
2	33.69ps	40.39ps
4	21.03ps	45.192ps

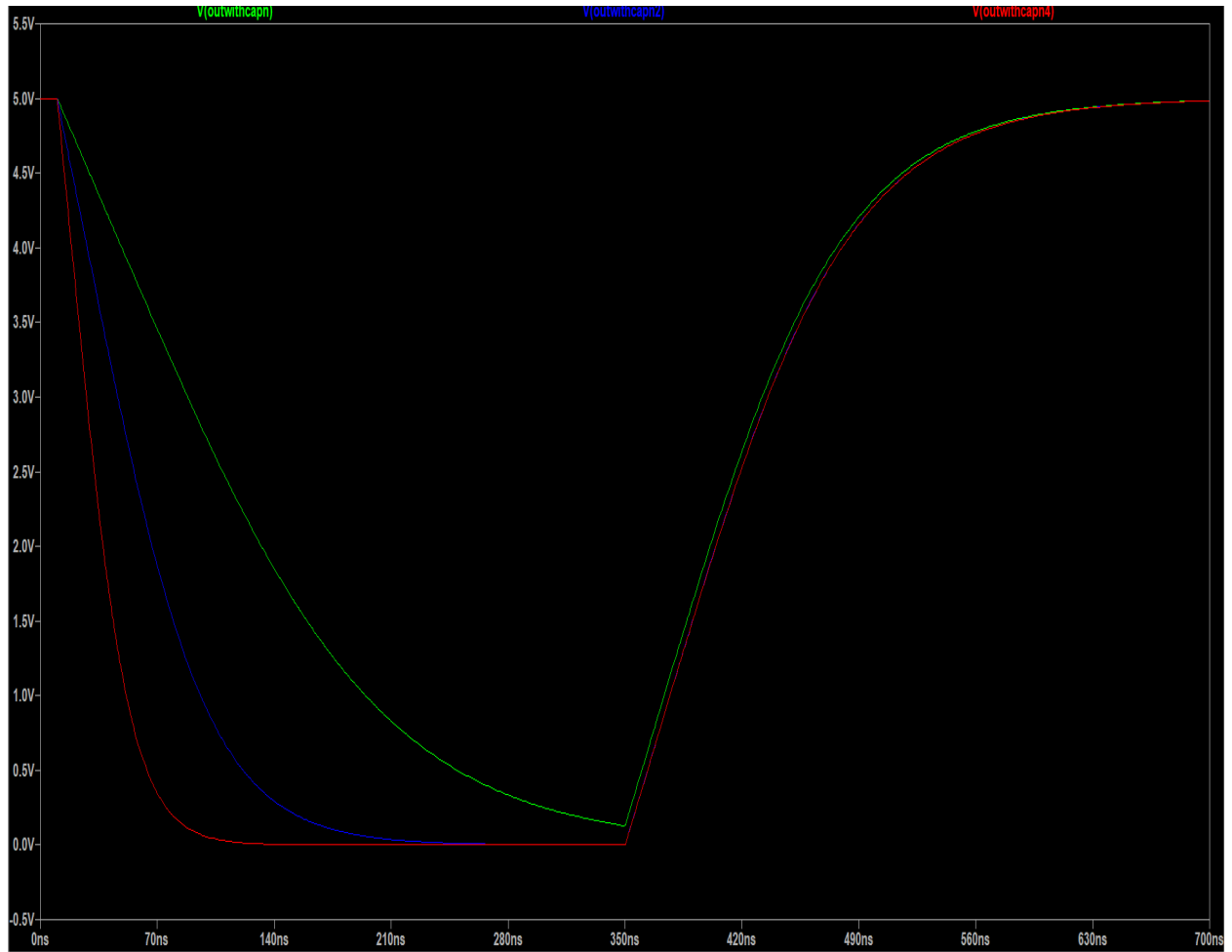


Fall and Rise time of Varying N with Capacitor

Size	Fall Time- n with cap	Rise Time- n with cap
1	220.21ps	156.78ps
2	100.59ps	154.89ps
4	49.99ps	153.76ps

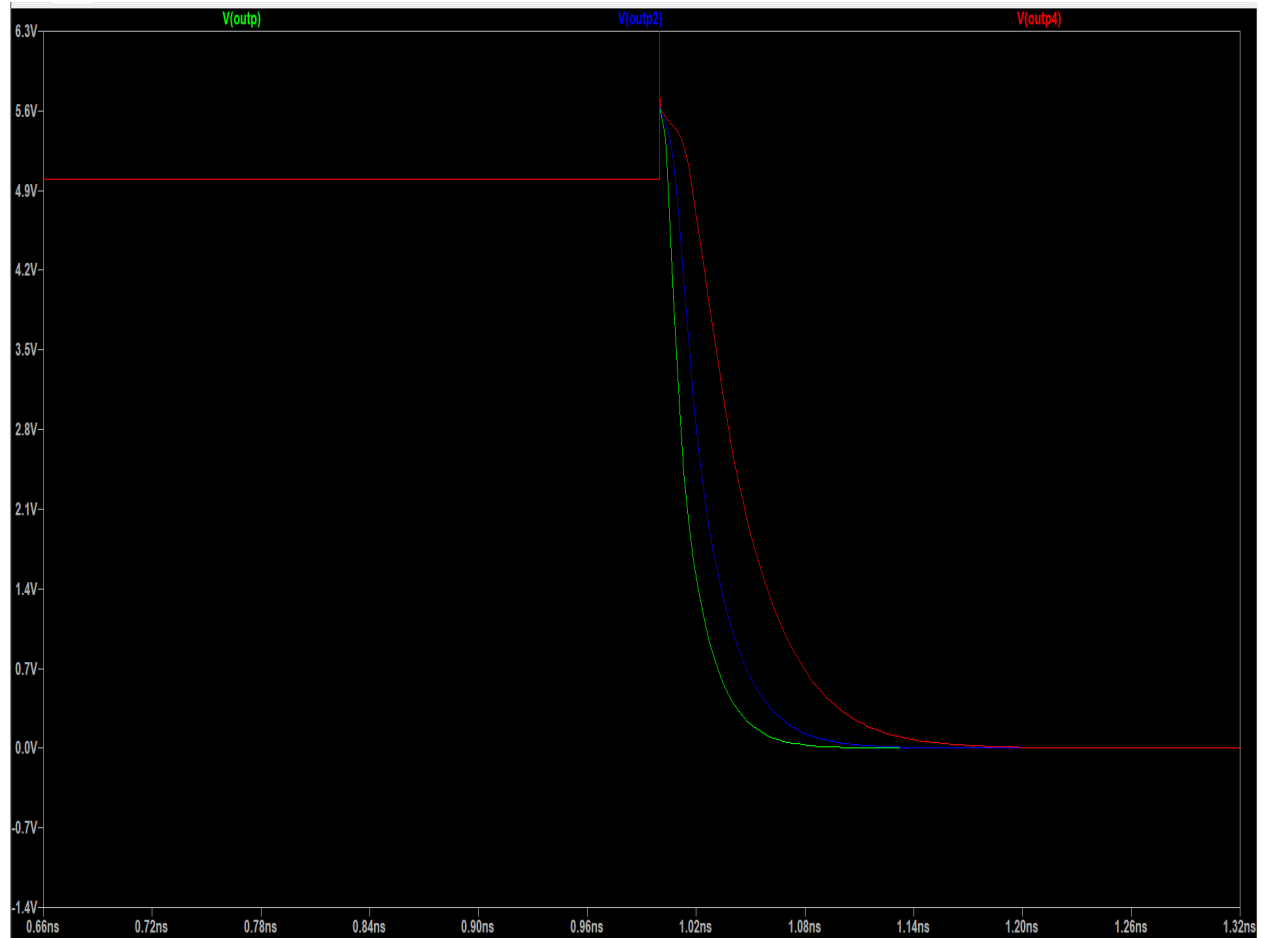


Fall time of Varying P without Capacitor

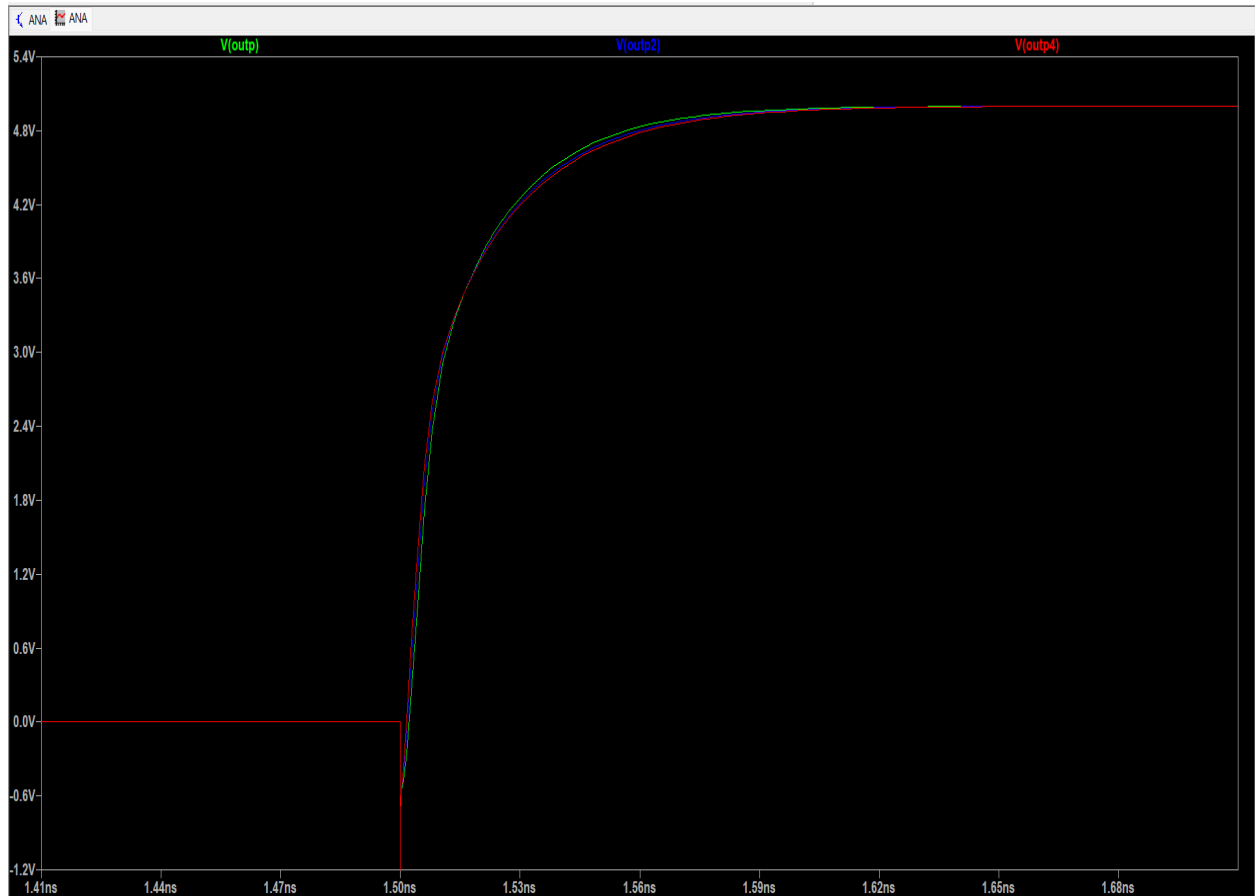


Rise time of Varying P without Capacitor

Size	Fall Time- p without cap	Rise Time- p without cap
1	30.798ps	39.190ps
2	43.00ps	38.404ps
4	67.159ps	38.766ps

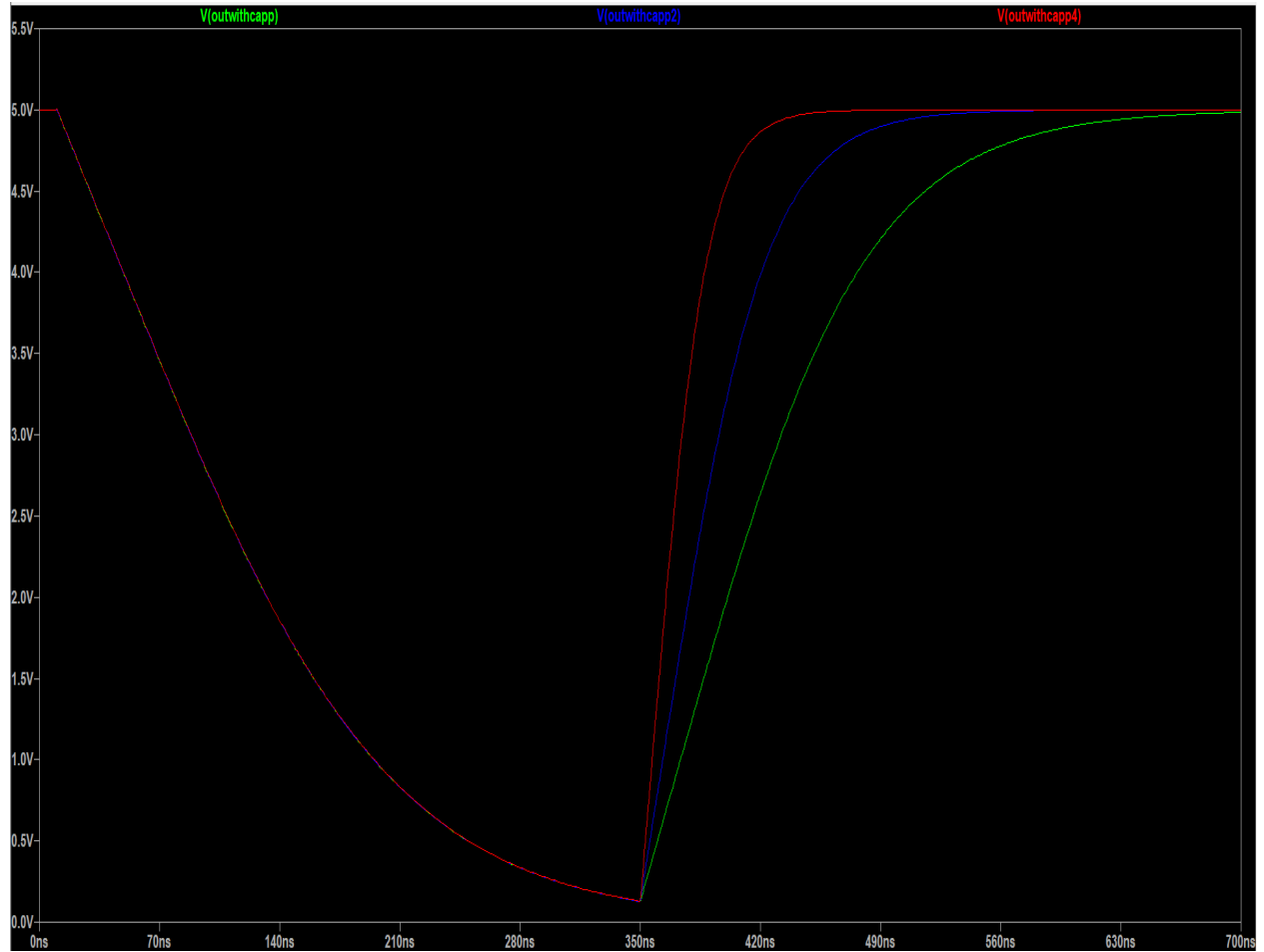


Fall and Rise time of Varying P with Capacitor

Size	Fall Time- n with cap	Rise Time- n with cap
1	220.21ps	156.77ps
2	219.08ps	86.27ps
4	218.7ps	45.78ps

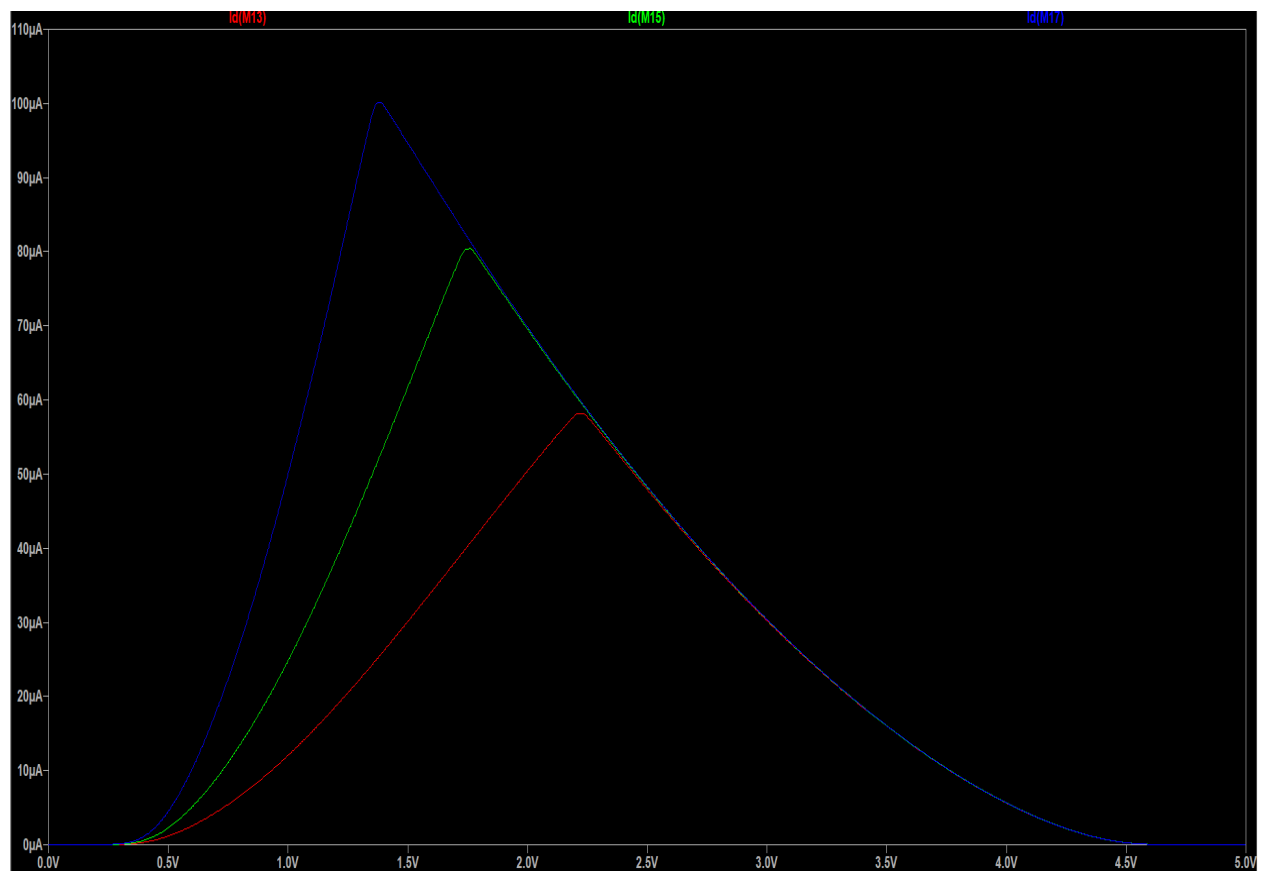

DC Current of Varying N

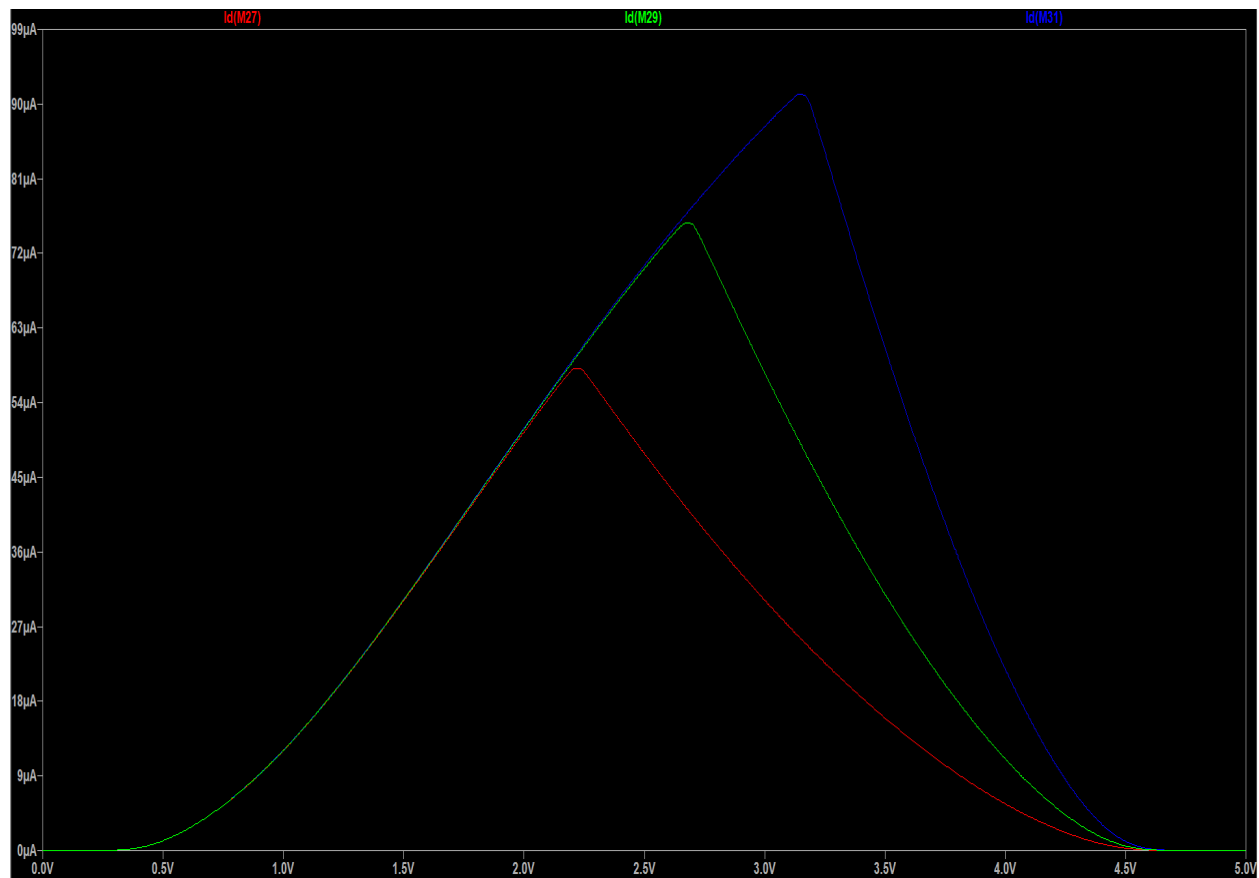

DC Current of Varying P

Power Calculations

Size	Avg Current	Static Power
1	21.92pA	109.6 pW
2	31.382pA	156.6pW
4	51.933pA	259.665pW